



# Digital Electronics™

## Final Examination

### Part A

Spring 2007

Student Name: \_\_\_\_\_

Date: \_\_\_\_\_

Class Period: \_\_\_\_\_

Total Points: \_\_\_\_\_ / 40

Converted Score: \_\_\_\_\_ / 50

## Multiple Choice


**Directions:** Select the letter of the response which best completes the item or answers the question. Then fill in the separate *Part A Answer Sheet*.

---

1. This task should be done before connecting an LED to a circuit.
- A. Place the LED directly across the power supply to see if the LED has not been damaged.
  - B. Place a capacitor in series with the LED to limit the maximum amount of current.
  - C. Use Ohm's Law to calculate the appropriate current limiting resistor to place in series with the LED.
  - D. Use Ohm's Law to calculate the appropriate current limiting resistor to place in parallel with the LED.
- 

2. Using scientific notation, which prefixes are used for values larger than a whole number?
- A. Milli, Micro, Kilo
  - B. Mega, Kilo, Giga
  - C. Nano, Pico, Giga
  - D. Milli, Nano, Mega
- 

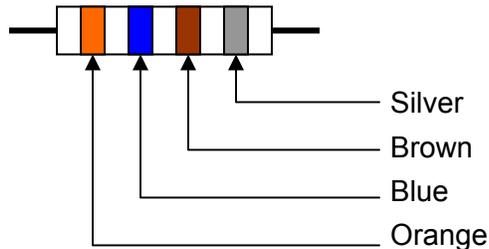3. What is the value of the resistor shown below?



- A.  $160\text{ K}\Omega \pm 10\%$
  - B.  $360\Omega \pm 5\%$
  - C.  $360\Omega \pm 10\%$
  - D.  $36\text{ K}\Omega \pm 5\%$
- 


4. What are the color bands for a  $56\text{ K}\Omega (\pm 5\%)$  resistor?
- A. YELLOW-GREEN-RED-SILVER
  - B. GREEN-BLUE-ORANGE-GOLD
  - C. BLUE-GRAY-GREEN-GOLD
  - D. GREEN-BLUE-ORANGE-SILVER
-

---

5. In a parallel circuit, you measure 20 mVolts across a  $400\ \Omega$  resistor. How much current is flowing through the resistor?

- A.** 8 Amps  
**B.** 5 mAmps  
**C.** 500 mAmps  
**D.**  $50\ \mu$ Amps
- 

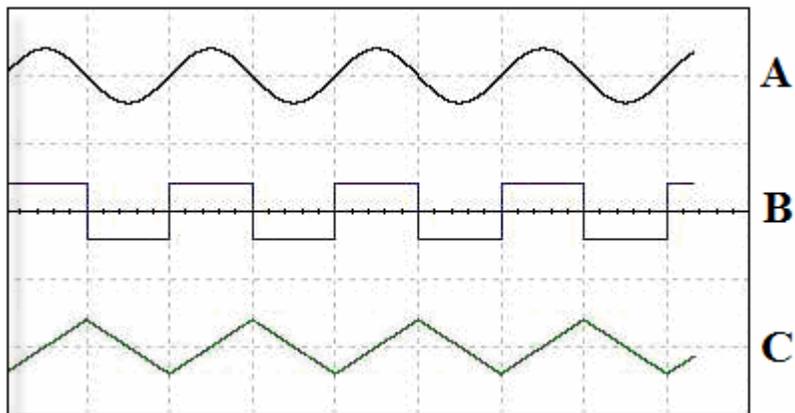6. Which of the waveforms shown below would be described as an analog triangle wave?



- A.** Waveform A  
**B.** Waveform B  
**C.** Waveform C  
**D.** None of the above
- 

7. What is the binary equivalent to the decimal number  $13_{10}$ ?

- A.**  $1101_2$   
**B.**  $0111_2$   
**C.**  $1011_2$   
**D.**  $1001_2$
- 





8. What is the hexadecimal equivalent to the binary number  $1010_2$ ?

- A.**  $5_H$   
**B.**  $A_H$   
**C.**  $10_H$   
**D.**  $2_H$
-

---

9. The truth-table shown below represents which of the following gates?





X	Y	Z
0	0	0
0	1	1
1	0	1
1	1	1

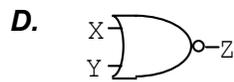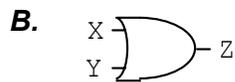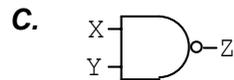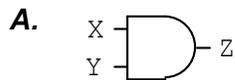

---

10. The truth-table shown below represents which of the following gates?

X	Y	Z
0	0	1
0	1	1
1	0	1
1	1	0

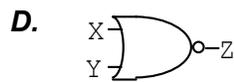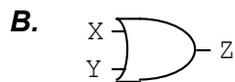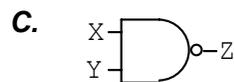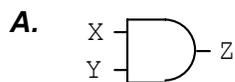

---

11. The gate shown below is represented by which of the following truth-tables?



**A.**

X	Y	Z
0	0	0
0	1	0
1	0	0
1	1	1

**C.**

X	Y	Z
0	0	0
0	1	1
1	0	1
1	1	1

**B.**


X	Y	Z
0	0	1
0	1	1
1	0	1
1	1	0

**D.**

X	Y	Z
0	0	1
0	1	0
1	0	0
1	1	0

---

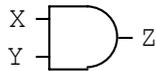12. The gate shown below is represented by which of the following truth-tables?



**A.**

X	Y	Z
0	0	0
0	1	0
1	0	0
1	1	1

**C.**

X	Y	Z
0	0	0
0	1	1
1	0	1
1	1	1

**B.**

X	Y	Z
0	0	1
0	1	1
1	0	1
1	1	0

**D.**

X	Y	Z
0	0	1
0	1	0
1	0	0
1	1	0

---

13. Which of the following is a rule of Boolean algebra?

**A.**  $X \bullet \bar{X} = \bar{X}$

**C.**  $X + \bar{X} = 0$

**B.**  $X \bullet X = X$

**D.**  $X + X = 1$

---

14. Which of the following is an example of Distributive Law of Boolean algebra?

**A.**  $X(YZ) = (XY)Z$

**C.**  $XY = YX$

**B.**  $X + XY = X$

**D.**  $X(Y + Z) = XY + XZ$

---

15. Which of the following is the simplified equivalent for the Boolean equation shown?

$$F_{15} = XY + X\bar{Y}$$

**A.**  $F_{15} = XY$

**C.**  $F_{15} = X\bar{Y}$

**B.**  $F_{15} = X$

**D.**  $F_{15} = Y$

---

16. Which of the following equations is the *un-simplified* Sum-Of-Products equation for the truth table shown?

X	Y	Z	F <sub>16</sub>
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	0

**A.**  $F_{16} = \bar{X}\bar{Y}Z + \bar{X}Y\bar{Z} + XY\bar{Z}$


**C.**  $F_{16} = \bar{X}\bar{Y}Z + \bar{X}\bar{Y}Z + XY\bar{Z}$

**B.**  $F_{16} = \bar{X}\bar{Y}Z + \bar{X}Y\bar{Z} + X\bar{Y}Z$

**D.**  $F_{16} = X\bar{Y}\bar{Z} + \bar{X}Y\bar{Z} + XY\bar{Z}$

---

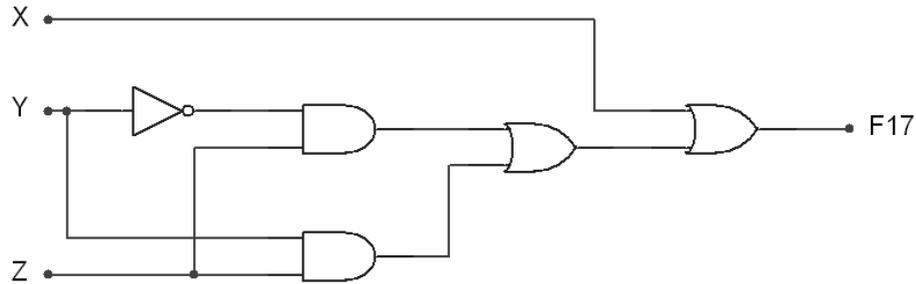17. Which of the following un-simplified Boolean expressions represent the logic circuit shown below?



- |  |  |
|--|--|
| <b>A.</b> $F_{17} = X + \bar{Y}Z + \bar{Y}\bar{Z}$ | <b>C.</b> $F_{17} = X + Y\bar{Z} + YZ$       |
| <b>B.</b> $F_{17} = X + \bar{Y}Z + YZ$             | <b>D.</b> $F_{17} = \bar{X} + \bar{Y}Z + YZ$ |

18. Which of the following is a correct DeMorgan's Identity?

- |   |   |
|---|---|
| <b>A.</b> $\overline{XY} = \bar{X} \cdot \bar{Y}$ | <b>C.</b> $\overline{XY} = \bar{X} + \bar{Y}$ |
| <b>B.</b> $\overline{XY} = X \cdot Y$             | <b>D.</b> $\overline{XY} = X + Y$             |

19. Which of the following is the simplified equivalent for the Boolean equation shown?

$$F_{19} = \overline{\overline{X} \overline{Y}}$$

- |                                  |                                  |
|----------------------------------|----------------------------------|
| <b>A.</b> $F_{19} = \bar{X}Y$    | <b>C.</b> $F_{19} = X\bar{Y}$    |
| <b>B.</b> $F_{19} = X + \bar{Y}$ | <b>D.</b> $F_{19} = \bar{X} + Y$ |

20. Which of the following K-Maps has the 1's & 0's properly placed for the function  $F_{20}$  ?

W	X	Y	Z	$F_{20}$
0	0	0	0	0
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1

**A.**

	$\bar{W}\bar{X}$	$\bar{W}X$	$WX$	$W\bar{X}$
$\bar{Y}\bar{Z}$	0	0	1	1
$\bar{Y}Z$	0	1	0	1
$YZ$	1	1	0	0
$Y\bar{Z}$	0	0	1	0

**C.**

	$\bar{W}\bar{X}$	$\bar{W}X$	$WX$	$W\bar{X}$
$\bar{Y}\bar{Z}$	0	0	1	0
$\bar{Y}Z$	0	1	1	0
$YZ$	1	0	0	1
$Y\bar{Z}$	1	1	0	0

**B.**


	$\bar{W}\bar{X}$	$\bar{W}X$	$WX$	$W\bar{X}$
$\bar{Y}\bar{Z}$	0	0	0	1
$\bar{Y}Z$	0	1	0	1
$YZ$	1	1	0	0
$Y\bar{Z}$	1	0	1	0

**D.**

	$\bar{W}\bar{X}$	$\bar{W}X$	$WX$	$W\bar{X}$
$\bar{Y}\bar{Z}$	0	0	0	1
$\bar{Y}Z$	0	1	0	1
$YZ$	1	0	1	0
$Y\bar{Z}$	1	1	0	0

21. Which of the following logic circuits correctly implements the Boolean equation?

$$F_{21} = \bar{Y}Z + Y\bar{Z}$$

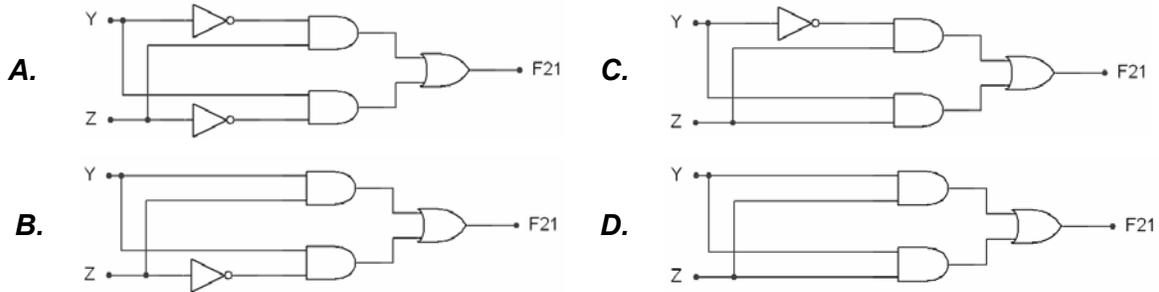

22. Which of the following K-maps is grouped properly and will result in the simplest solution?

	$\bar{X}\bar{Y}$	$\bar{X}Y$	$XY$	$X\bar{Y}$
$\bar{Z}$	1	0	X	0
Z	1	X	X	1

**A.**

	$\bar{X}\bar{Y}$	$\bar{X}Y$	$XY$	$X\bar{Y}$
$\bar{Z}$	1	0	X	0
Z	1	X	X	1

**B.**

	$\bar{X}\bar{Y}$	$\bar{X}Y$	$XY$	$X\bar{Y}$
$\bar{Z}$	1	0	X	0
Z	1	X	X	1

**C.**

	$\bar{X}\bar{Y}$	$\bar{X}Y$	$XY$	$X\bar{Y}$
$\bar{Z}$	1	0	X	0
Z	1	X	X	1

**D.**

	$\bar{X}\bar{Y}$	$\bar{X}Y$	$XY$	$X\bar{Y}$
$\bar{Z}$	1	0	X	0
Z	1	X	X	1




23. Which Boolean equation is in Product-Of-Sums form?

- A.**  $F_{23} = XY\bar{Z} + X\bar{Y} + XYZ$       **C.**  $F_{23} = (X + Y)(X + Z)(\bar{Y} + Z)$
- B.**  $F_{23} = X\bar{Y}\bar{Z} + Z(X + Y)$       **D.**  $F_{23} = X(Y + Z)(\bar{Y} + Z)$

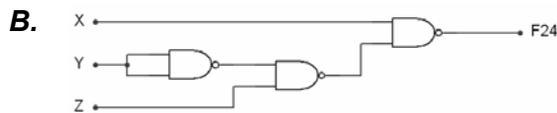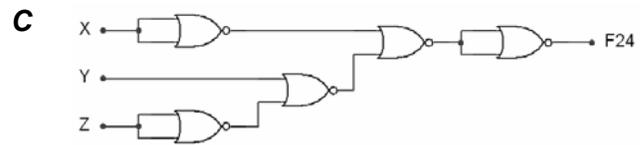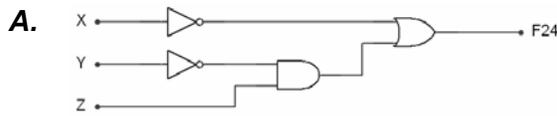24. The three circuits shown below all implement the logic equation:


$$F_{24} = \bar{X} + \bar{Y} Z$$

Of these circuits, which one would require the least number of IC chips?



**D.** All of the above

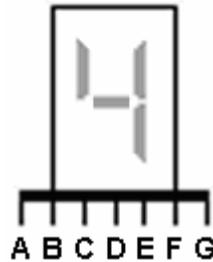25. What logic values need to be placed on the inputs (a) through (g) of the common-cathode seven-segment in order to display the number 4?



**A.**

A	B	C	D	E	F	G
1	0	0	1	1	0	1

**C.**

A	B	C	D	E	F	G
0	1	1	0	0	1	1

**B.**

A	B	C	D	E	F	G
0	1	0	0	1	1	0

**D.**

A	B	C	D	E	F	G
0	0	1	1	1	0	1

26. When typing the Boolean expression  $F = \bar{X} + \bar{Y} Z$  into the WinCupl program, which of the following expressions would be entered?


**A.**  $F = !X \# !Y \& Z;$

**C.**  $F = \text{not}(X) \text{ or } \text{not}(Y) \text{ and } Z;$

**B.**  $F = !X + !Y Z;$

**D.**  $F = X' + Y'Z;$

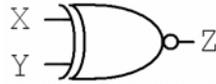27. The gate shown below is represented by which of the following truth-tables?



**A.**

X	Y	Z
0	0	1
0	1	0
1	0	0
1	1	1

**C.**

X	Y	Z
0	0	1
0	1	0
1	0	1
1	1	0





**B.**

X	Y	Z
0	0	0
0	1	1
1	0	1
1	1	0

**D.**

X	Y	Z
0	0	0
0	1	1
1	0	0
1	1	1

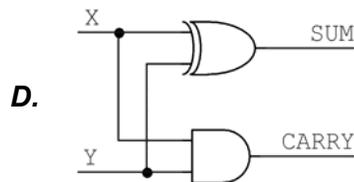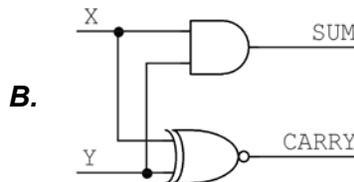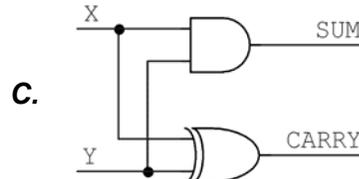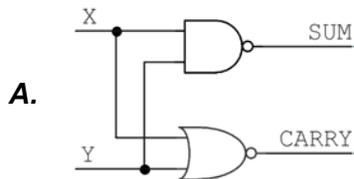28. Which of the following circuits is a half-adder?




29. How are the Q and  $\bar{Q}$  outputs of a flip flop affected by setting the active high asynchronous PRESET input to a logic one?

- A.** No change.
- B.** Q = 1 and  $\bar{Q}$  = 0
- C.** Q = 0 and  $\bar{Q}$  = 1
- D.** Q = 1 and  $\bar{Q}$  = 1


---

30. Which of the devices shown below is a Negative Edge Triggered J/K Flip-Flop?


**A.**

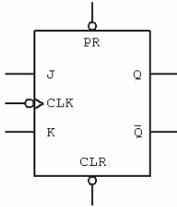


**C.**

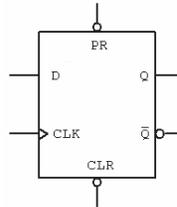

**B.**

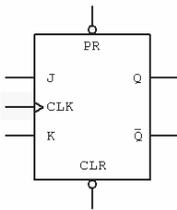

**D.**

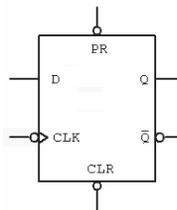

---

31. How many flip-flops are required to implement a divide-by-8 circuit?

**A.** 1


**C.** 3

**B.** 2

**D.** 4

---

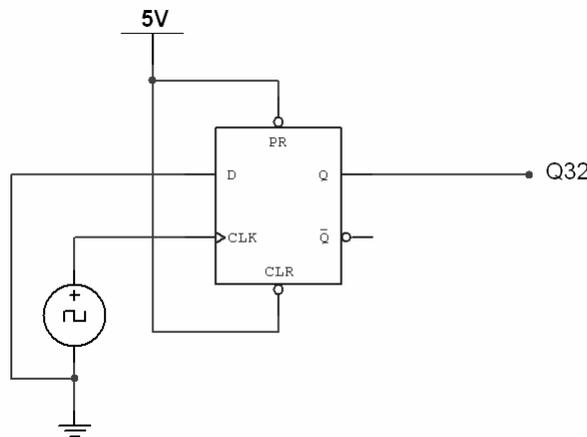32. Regardless of its current value, what will happen to the output **Q32** on the next clock pulse?



**A.** Q32 will be low.


**C.** Q32 will toggle.

**B.** Q32 will be high.

**D.** Q32 will not change.

---

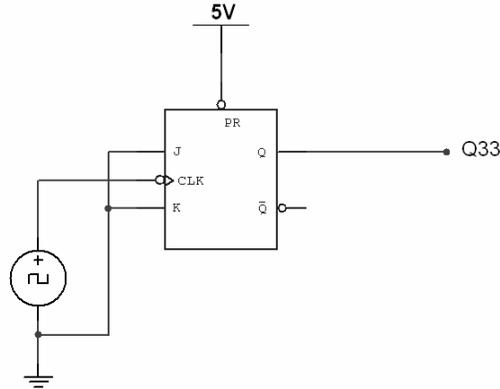
33. Regardless of its current value, what will happen to the output **Q33** on the next clock pulse?



- A. Q33 will be low.
- B. Q33 will be high.
- C. Q33 will toggle.
- D. Q33 will not change.

---

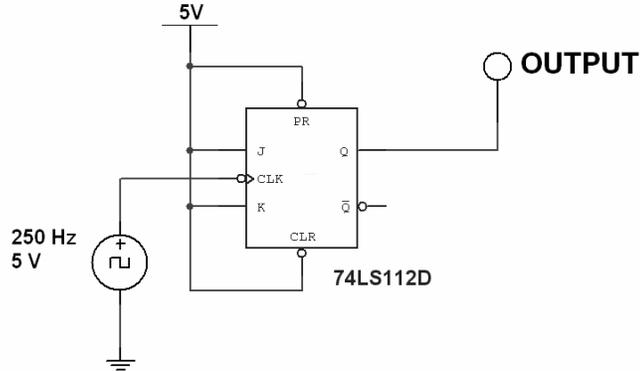
34. Determine the frequency of the signal **OUTPUT** for the circuit shown below.



- A. 250 Hz.
- B. 125 Hz.
- C. 500 Hz.
- D. 1 KHz.

---

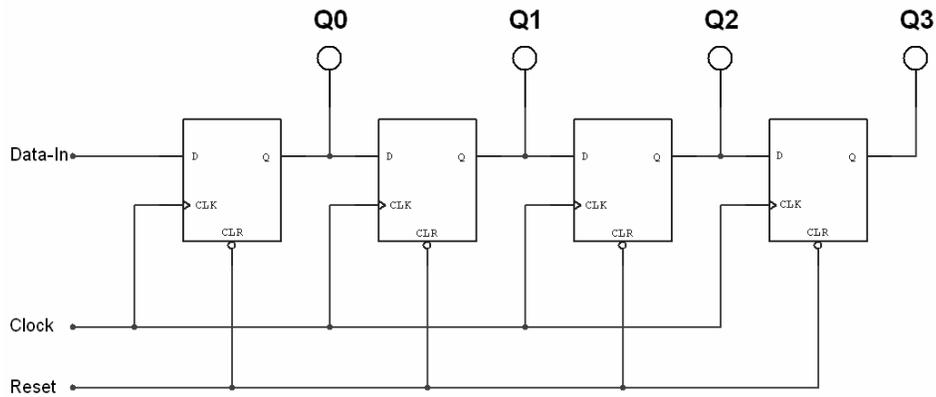35. What type of shift register is shown below?



- A.** Serial-In / Serial-Out                      **C.** Parallel-In / Parallel-Out  
**B.** Serial-In / Parallel-Out                    **D.** Parallel-In / Serial-Out


---

36. Asynchronous counters are also called \_\_\_\_\_.

- A.** glitch counters.                              **C.** ripple counters.  
**B.** pulse wave counters.                      **D.** step counters.


---

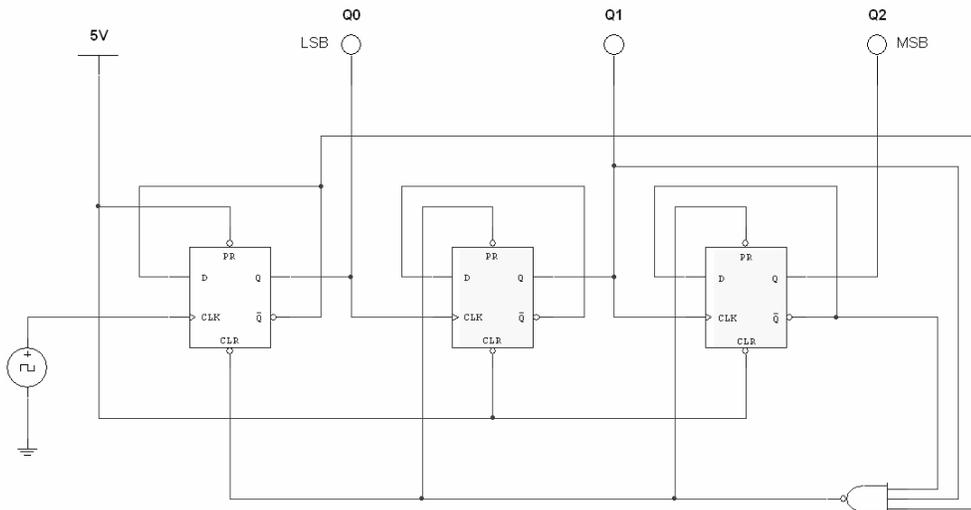37. What is the count range of the 3-bit asynchronous shown below?



- A.** 2 to 6    **C.** 6 down to 2  
**B.** 3 to 6    **D.** 6 down to 3

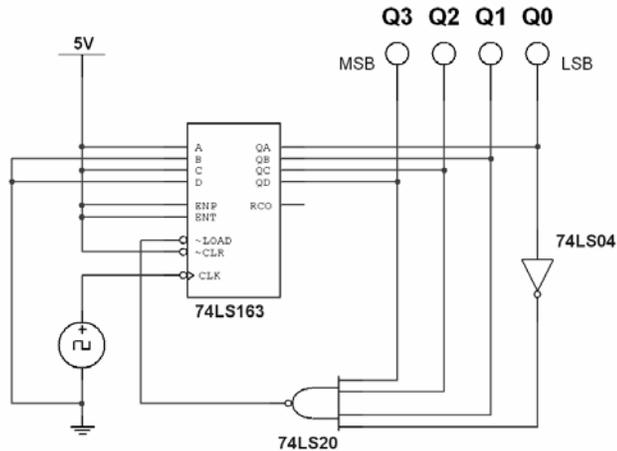38. What is the count range of the 4-bit synchronous shown below?



- A. 5 to 14
- B. 5 to 15
- C. 4 to 14
- D. 4 to 15

39. When comparing TTL logic gates to CMOS gates, which of the following statements is true?

- A. TTL gates use less power than CMOS gates.
- B. TTL have a higher noise margin than CMOS gates.
- C. TTL are faster than CMOS gates.
- D. TTL gates are more sensitive to static electricity than CMOS gates.

40. Propagation delay is \_\_\_\_\_.

- A. a measure of the ability of a logic gate to drive further logic gates.
- B. the difference in chip temperature from when the power is off to when the power is on.
- C. the difference between what a logic gate outputs as a valid logic voltage and what the input of the next gates expects to see as a valid logic voltage.
- D. the time required for a signal to travel from the input of a logic gate to the output.