

Semester 1 Final Study Guide

Digital Electronics

Directions: Complete all of the work in your engineering notebook. Completion of this review study guide will count like an engineering notebook check worth 30 points.

Semester 1 Outline:

A. Scientific Notation vs. Engineering Notation

- Explain how to write numbers in scientific notation.
- Explain how to write numbers in engineering notation.
- What are the SI prefixes that you will need to memorize in order to write numbers in Scientific notation or engineering notation?

B. Component Identification: Resistors and Capacitors

- What is a resistor?
- How do you determine the nominal value for a resistor?
- What is a capacitor?
- How do you determine the nominal value for a capacitor?

C. Circuit Theory Laws:

- What is current, voltage, and resistance?
- What is Ohm's Law?
- What is the difference between Parallel Circuits and Series Circuits?

D. Analog vs. Digital Signals

- What is a logic level?
- What is an analog Signal?
- What is a digital Signal?

E. Number Systems

- Binary
 - i. Why do engineers use the binary system to express numbers?
 - ii. How do you convert from decimal → binary and from binary → decimal?
- Octal
 - i. How do you convert from octal → Decimal and from decimal → octal?
- Hexadecimal
 - i. How do you convert from hexadecimal → decimal and from decimal → hexadecimal?

F. Combinational Design Logic: AOI

- What is AOI Logic? What do each of the gates represent in AOI logic?
- How do you write a truth table if given 2 inputs, 3 inputs, etc.?
- How do you find minterms from a truth table?
- How do you write a logic expression from minterms or from a truth table?
- How do you draw circuits from logic expressions?
- How do you derive a truth table from an existing circuit using "method 1"?
- How do you derive a truth table from an existing circuit using "method 2"?

G. Alternative Combinational Design Logic:

- NAND Logic
 - i. What is NAND logic? What do each of the gates represent in NAND logic?
- NOR Logic
 - i. What is NOR logic? What do each of the gates represent in NOR logic?
- What are the pros/cons of using NAND/NOR logic over AOI logic?

H. Circuit Simplification Techniques

- i. Boolean Algebra
 - Explain how to simplify logic expressions using Boolean Algebra.
- ii. DeMorgan's Theorems
 - Explain how to simplify logic expressions using DeMorgan's Theorems.
- iii. K-Mapping
 - Explain how to simplify logic expressions using the K-mapping technique.


I. Seven Segment Displays

- What does each "segment" represent?
- What is the different between a Common Anode and a common cathode?
- Explain how you could display any number using a seven segment display.

Example Final Questions

1. Write the following numbers in engineering notation and scientific notation.
 - a) 0.00033000
 - b) 100300
2. Using the resistor color code chart determine the nominal resistance value for a resistor with the following colors:
 - a) Violet/Black/Blue/Gold
 - b) Gray/Yellow/Green/Silver
3. Use the following circuit to calculate each of the following: (make sure to include units!)
 - a) Calculate the total resistance, total current, and the total voltage
 - b) Calculate the current flowing through each component
 - c) Calculate the voltage across each component
 - d) Is this a parallel or series circuit?
4. Convert the following binary numbers into decimal.
 - a) 101011_2
 - b) 10_2
 - c) 100_2
 - d) 110011_2

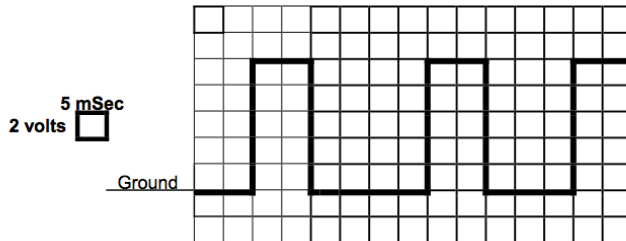5. Convert the following decimal numbers into binary
- 17_{10}
 - 189_{10}
 - 11_{10}
 - 100_{10}
6. For the square wave shown below, determine its (a) period, (b) frequency, (c) duty cycle, and (d) amplitude. Be sure to show correct units.



- Period
- Frequency
- Duty Cycle
- Amplitude

7. Determine the minterms from the following truth table and then write the logic expression

X	Y	Z	F
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

8. Use the following truth table to answer the questions below

P	Q	R	F ₃
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

Write the Logic Expression from the Truth Table above.

- Draw the circuit for the following Logic Expression that you wrote using AOI logic
- Check to make sure that your circuit is correct using method 1 or method 2
- Redraw the circuit using NAND logic and simplify
- Redraw the circuit using NOR logic and simplify

9. Write the most simplified logic expression using the K-mapping technique

a)

A	B	F ₁
0	0	0
0	1	1
1	0	1
1	1	1

F₁ = _____

b)

A	B	C	F ₂
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

F₂ = _____

c)

A	B	C	D	F ₃
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1

F₃ = _____

10. Use the following expression to answer the questions below:

$$F_1 = A \bar{C} + \bar{A} C + A \bar{B} C$$

- a) Draw the above circuit using the fewest possible gates using AOI logic.
- b) Draw the above circuit using only 2 input gates using AOI logic.

11. Simplify the following logic expressions using Boolean and DeMorgan's Theorems

a)

$$F_4 = PS + P\bar{Q}\bar{S} + PQS$$

b)

$$F_2 = \overline{(\bar{X} + Z)(\bar{X}Y)}$$

12. Convert the following decimal numbers to octal and hexadecimal.

- a) 10_{10}
- b) 100_{10}
- c) 3345_{10}

13. Convert the following octal numbers to decimal numbers.

- a) 367_8
- b) 100_8

14. Convert the following hexadecimal numbers to decimal numbers.

- a) $2A3_{16}$
- b) $1AB3_{16}$

15. From the following logic expression create the truth table.

$$F_1 = \bar{A}\bar{B}\bar{C}D + B\bar{C}\bar{D} + A\bar{B}$$

16. From the following circuit derive the logic expression using test points from "method 1" or "method 2".

